

## **LAB 0**

# **Systolic Array for Applying Matrix Multiplication**

**By: Youssef Sameh Fawzy**

**Instructor: Ahmed Abdelsalam**

---

## **Content:**

### **1 – Architecture**

A short abstract about how our systolic array works.

### **2 – RTL Codes**

Contains a code for 3x3 fixed systolic array that I implemented at first to apply on what I learned and a parameterized systolic array that takes N\_SIZE and DATA\_WIDTH.

### **3 – Simulation**

Contains a code for the TB and running it and viewing the wave forms

### **4 – What is missing?**

Contains the things that we failed to handle correctly in the RTL code.

### **5 – Vivado Elaboration**

Contains schematic of the RTL.

## **1- Architecture:**


**First , We need to understand how our Systolic array works.**

**Every clock cycle it takes a column from Matrix A , and a row from Matrix B and enter them on a grid of PEs (processing element). Every PE makes it's calculation then pass it's input to the following PE. The A input goes from left to right and that of B from up to down. The input A or B will pass on a register depending on the row or coloumn it goes in. The first part of the input goes directly to the PE but the next one will pass through a register first so it will be delayed a cycle.This will insure that the previous PE has completed its operation and passed the output completely.**

**The output is taken on Matrix C as rows, when the first row is ready it gets to the output, and when the second row is ready it overwrites the previous row. We have a signal called "valid\_out" that indicates when the output is available to take.**

**There is another signal called "valid\_in" that indicates whether we will take the input from matrix A and B or not.**

 **We have an internal counter that will help us indicating when the valid\_out will be ready.**



This is a visualization of how it works , but with each PE has output connected to the right PE and down PE to pass the value of A and B.

## 2-RTL Codes:

At first , I did a fixed 3x3 Systolic array to implement on what I have learned.

I noticed blocks being used a lot in the implementation which are the registers and the Processing elements so I did them in a separate modules.

```

module PE#(parameter data_size=8)(
  input wire rst_n,clk,
  input wire [data_size-1:0] in_a,in_b,
  output reg [2*data_size-1:0] out_c,
  output reg [data_size-1:0] out_a,out_b
);
always @(posedge clk)begin
  if(!rstn_n) begin
    out_a <= 0;
    out_b <= 0;
    out_c <= 0;
  end else begin
    out_c <= out_c + in_a*in_b;
    out_a <=in_a;
    out_b <=in_b;
  end
end
endmodule

```

The PE module simply took input from the left and from up and multiply them then adds it to out\_c which accumulate each cycle and that will be the out of this element of the matrix.

```

module DFF #(parameter data_size = 8)(
  input clk,
  input rst_n,
  input [data_size-1:0] d,
  output reg [data_size-1:0] q
);
always @(posedge clk) begin
  if (!rst_n) begin
    q <= 0;
  end else begin
    q <= d;
  end
end
endmodule

```

The register module simply takes d and after a clk cycle it passes it to q, this will delay the input as we expects.

Then we will instantiate them all in the systolic array module.

**Systolic3x3:**

```
fixed3x3systolic.sv > systolic3x3
1  module systolic3x3#(parameter data_size=8)(
2  input clk,rstn_n,
3  input [data_size*3-1:0] matrix_a_in,
4  input [data_size*3-1:0] matrix_b_in,
5  output reg valid_out,
6  output reg [data_size*3*2-1:0] matrix_c_out
7  );
8      reg [3:0] counter1;
9  always @(posedge clk) begin
10     if (!rstn_n) begin
11         counter1 <= 0;
12     end else begin
13         if (counter1 < 7) counter1 <= counter1 + 1;
14     end
15 end
16
17 always @(posedge clk) begin
18     if (!rstn_n)
19         valid_out <= 0;
20     else begin
21         valid_out <= (counter1 >= 4 && counter1 <= 6);
22     end
23 end
24
```

First we declare the inputs and we initiate a counter.

As it is a 3x3 array we already know when the output will be ready at cycle 5,6 and 7 so we made valid\_out = 1 at that time.

```

//Registers to delay the input
DFF dff1(.clk(clk), .rst_n(rstn_n), .d(matrix_a_in[data_size*2-1:data_size]), .q(a2_reg));
DFF dff2(.clk(clk), .rst_n(rstn_n), .d(matrix_a_in[data_size*3-1:data_size*2]), .q(a3_reg1));
DFF dff3(.clk(clk), .rst_n(rstn_n), .d(a3_reg1), .q(a3_reg2));
DFF dff4(.clk(clk), .rst_n(rstn_n), .d(matrix_b_in[data_size*2-1:data_size]), .q(b2_reg));
DFF dff5(.clk(clk), .rst_n(rstn_n), .d(matrix_b_in[data_size*3-1:data_size*2]), .q(b3_reg1));
DFF dff6(.clk(clk), .rst_n(rstn_n), .d(b3_reg1), .q(b3_reg2));

wire [2*data_size-1:0] c1,c2,c3,c4,c5,c6,c7,c8,c9;
PE PE1 (.clk(clk), .rst_n(rstn_n), .in_a(matrix_a_in[data_size-1:0]), .in_b(matrix_b_in[data_size-1:0]), .out_a(a1to2), .out_b(b1to4),
.out_c(c1));
PE PE2 (.clk(clk), .rst_n(rstn_n), .in_a(a1to2), .in_b(b2_reg), .out_a(a2to3), .out_b(b2to5), .out_c(c2));
PE PE3 (.clk(clk), .rst_n(rstn_n), .in_a(a2to3), .in_b(b3_reg2), .out_a(), .out_b(b3to6), .out_c(c3));
PE PE4 (.clk(clk), .rst_n(rstn_n), .in_a(a2_reg), .in_b(b1to4), .out_a(a4to5), .out_b(b4to7), .out_c(c4));
PE PE5 (.clk(clk), .rst_n(rstn_n), .in_a(a4to5), .in_b(b2to5), .out_a(a5to6), .out_b(b5to8), .out_c(c5));
PE PE6 (.clk(clk), .rst_n(rstn_n), .in_a(a5to6), .in_b(b3to6), .out_a(), .out_b(b6to9), .out_c(c6));
PE PE7 (.clk(clk), .rst_n(rstn_n), .in_a(a3_reg2), .in_b(b4to7), .out_a(a7to8), .out_b(), .out_c(c7));
PE PE8 (.clk(clk), .rst_n(rstn_n), .in_a(a7to8), .in_b(b5to8), .out_a(a8to9), .out_b(), .out_c(c8));
PE PE9 (.clk(clk), .rst_n(rstn_n), .in_a(a8to9), .in_b(b6to9), .out_a(), .out_b(), .out_c(c9));

always @(*) begin
    case (counter1)
        5: begin
            matrix_c_out[2*data_size-1:0] = c1; matrix_c_out[data_size*4-1:2*data_size] = c2; matrix_c_out[data_size*6-1:data_size*4]
        end
        6: begin
            matrix_c_out[2*data_size-1:0] = c4; matrix_c_out[data_size*4-1:2*data_size] = c5; matrix_c_out[data_size*6-1:data_size*4]
        end
        7: begin
            matrix_c_out[2*data_size-1:0] = c7; matrix_c_out[data_size*4-1:2*data_size] = c8; matrix_c_out[data_size*6-1:data_size*4]
        end
    endcase
end

```

As we know it's a 3x3 we will only instantiate the number of DFF and PE we need , we made some wires called c from 1 to 9 to get the output on them till they are ready and we give them to the mat\_c\_out. At last as we know the output will be ready at cycle 5,6 and 7.


Then we used a tb and directed values we know the expect of them.

```

1  module test;
2
3      reg clk;
4      reg reset;
5  ✓ reg [23:0] matrix_a_in, matrix_b_in;
6      reg valid_in;
7
8  ✓ wire [47:0] matrix_c_out;
9
10
11     systolic3x3 uut (
12         .clk(clk),
13         .reset(reset),
14         .matrix_a_in(matrix_a_in),
15         .matrix_b_in(matrix_b_in),
16         .valid_out(valid_out),
17  ✓ .matrix_c_out(matrix_c_out)
18     );
19
20     initial begin
21  ✓ reset = 0;
22         matrix_a_in = 24'h000000; // Initialize to zero
23         matrix_b_in = 24'h000000; // Initialize to zero
24         @(posedge clk); reset = 1;
25  ✓ @(posedge clk); reset = 0;
26         matrix_a_in = 24'h070401; // Example values for matrix A
27         matrix_b_in = 24'h030102; // Example values for matrix B
28  ✓ @(posedge clk);
29         matrix_a_in = 24'h080502; // Example values for matrix A
30         matrix_b_in = 24'h070504; // Example values for matrix B
31         @(posedge clk);
32         matrix_a_in = 24'h090603; // Example values for matrix A
33         matrix_b_in = 24'h080906; // Example values for matrix B
34  ✓ @(posedge clk); // Clear valid input after processing
35         matrix_a_in = 24'h000000;
36         matrix_b_in = 24'h000000;
37
38         repeat(10) @(posedge clk); // Wait for some cycles to observe outputs
39
40
41     #100;
42     $stop;
43     end
44

```

 We ran it and it gave us correct output with correct timing of valid\_out.



This is not enough as we ignored valid\_in and we need to parametrize the input array size



## Parameterized Systolic Array:

We will do the same as we did for the 3x3 but for every dimensions of the matrix.

```
parameterizedsystolic.sv > systolic_array
1  module systolic_array #(
2  parameter DATAWIDTH = 16,
3  parameter N_SIZE = 5)(
4  input clk,rst_n,valid_in,
5  input [N_SIZE*DATAWIDTH-1:0] matrix_a_in,matrix_b_in,
6  output reg valid_out,
7  output reg [N_SIZE*2*DATAWIDTH-1:0] matrix_c_out
8  );
9
10 reg [N_SIZE] clk_counter;
11 always@(posedge clk or negedge rst_n) begin
12     if(!rst_n) begin
13         clk_counter <= 0;
14     end
15     else clk_counter <= clk_counter + 1;
16 end
17
```

First we declared the inputs and outputs as specified then we made a counter the counts the clock cycles as it will be important in next operations.

```

wire [DATAWIDTH-1:0] a_reg[0:N_SIZE-1];
wire [DATAWIDTH-1:0] b_reg[0:N_SIZE-1];
assign a_reg[0]= (valid_in) ? matrix_a_in[DATAWIDTH-1 : 0] : {DATAWIDTH{1'b0}};
assign b_reg[0]= (valid_in) ? matrix_b_in[DATAWIDTH-1 : 0] : {DATAWIDTH{1'b0}};

genvar i, j;
generate
    for (i = 1; i < N_SIZE; i = i + 1) begin : A_PIPE
        wire [DATAWIDTH-1:0] a_input = (valid_in) ? matrix_a_in[(i+1)*DATAWIDTH-1 -: DATAWIDTH] : {DATAWIDTH{1'b0}};
        DFF #(.DATAWIDTH(DATAWIDTH), .NUM_DFF(i)) A(
            clk,
            rst_n,
            a_input,
            a_reg[i]
        );
    end

    for (j = 1; j < N_SIZE; j = j + 1) begin : B_PIPE
        wire [DATAWIDTH-1:0] b_input = (valid_in) ? matrix_b_in[(j+1)*DATAWIDTH-1 -: DATAWIDTH] : {DATAWIDTH{1'b0}};
        DFF #(.DATAWIDTH(DATAWIDTH), .NUM_DFF(j)) B(
            clk,
            rst_n,
            b_input,
            b_reg[j]
        );
    end
endgenerate

```

We now want to parameterize the number of registers before each PE on the first row and coloumn. For a\_reg[0] and b\_reg[0] it will be assigned directly as the least part of the matrixA and matrixB inputs as we need no regs for them to enter the PE.

Number of registers is a function in N\_SIZE, so we made a variable i and for each increament we increase the number of DFF by 1.

If valid\_in is 1 all regs will take its part of the input but if not they will take a 0.

```

module DFF #(parameter DATAWIDTH = 16, NUM_DFF = 1) (
    input clk,
    input wire rst_n,
    input wire [DATAWIDTH-1:0] d,
    output wire [DATAWIDTH-1:0] q
);
    reg [DATAWIDTH-1:0] stage_array [0:NUM_DFF-1];
    integer i;

    always @(posedge clk or negedge rst_n) begin
        if (!rst_n) begin
            for (i = 0; i < NUM_DFF; i = i + 1)
                stage_array[i] <= '0;
        end else begin
            stage_array[0] <= d;
            for (i = 1; i < NUM_DFF; i = i + 1)
                stage_array[i] <= stage_array[i - 1];
        end
        assign q = stage_array[NUM_DFF - 1];
    end
endmodule

```

That's the DFF module we used.

It's idea is that we put the input d in an array and we shift it each clock cycle to the left till we reach the value of NUM\_DFF we want and the q output will take it after NUM\_DFF clk cycle.

```

wire [2*DATAWIDTH-1:0] c [0:N_SIZE-1][0:N_SIZE-1];
wire [DATAWIDTH-1:0] a_bet_pe [0:N_SIZE-1][0:N_SIZE-1];
wire [DATAWIDTH-1:0] b_bet_pe [0:N_SIZE-1][0:N_SIZE-1];

generate
    for (i = 0; i < N_SIZE; i = i + 1) begin
        for (j = 0; j < N_SIZE; j = j + 1) begin
            PE #(.data_size(DATAWIDTH)) pe(clk,rst_n,(j == 0) ? a_reg[i] : a_bet_pe[i][j-1] ,(i == 0) ? b_reg[j] : b_bet_pe[i-1][j]
            , c[i][j], a_bet_pe[i][j],b_bet_pe[i][j]);
        end
    end
endgenerate

```

We first declared the internal wires between every pe and each other and the output of it is assigned to a wire C. a\_bet\_pe and b\_bet\_pe are 2-D to represent the internal wires between PE.

If the pe is in the first coloumn we take a\_reg[i] directly but if not we take from the previous a\_bet\_pe and the same for B if it's first row we take from b\_reg and if not we take from the previous(upove) b\_between\_pe.

```
module PE#(parameter data_size=16)(
  input wire clk,rst_n,
  input wire [data_size-1:0] in_a,in_b,
  output reg [2*data_size-1:0] out_c,
  output reg [data_size-1:0] out_a,out_b
);
always @(posedge clk or negedge rst_n)begin
  if(!rst_n) begin
    out_a <= 0;
    out_b <= 0;
    out_c <= 0;
  end else begin
    out_c <= out_c + in_a*in_b;
    out_a <=in_a;
    out_b <=in_b;
  end
end
endmodule
```

This is the PE module. We take the 2 inputs a and b and multiply it then we accumulate it to the value of out\_c we have already. Then we pass the 2 inputs to the following PE.

```

integer out_col;
✓ always @(*) begin
✓   if (clk_counter >= 2*N_SIZE - 1 && clk_counter <= 3*N_SIZE - 2) begin
       valid_out = 1'b1;
       for (out_col = 0; out_col < N_SIZE; out_col = out_col + 1) begin
✓         matrix_c_out[(out_col+1)*2*DATAWIDTH-1 -: 2*DATAWIDTH] =
           c[clk_counter - (2*N_SIZE - 1)][out_col];
       end
✓   end else begin
       matrix_c_out = 'b0;
       valid_out = 1'b0;
       end
end
end

```

Finally, We get the output, it's always expected that the output rows will be ready in every clk from the range between  $2*N\_SIZE-1$  to  $3*N\_SIZE-2$ . At  $clk\_counter = 2*N\_SIZE-1$  we will get row 1 till the final row will be ready at  $3*N\_SIZE-2$ .

The `matrix_c_out` will take the rows 1 by 1 from the C wires which is the output of every PE.

We make the rows fixed as it is always  $= clk\_counter - (2*N\_SIZE-1)$  and iterate through the coloumn.

`Matrix_C_out` will take all c from the row and put them from MSB to LSB.

We make `valid_out = 0` and reset the `matrix_c_out` after all the rows are got on the output.

---

### 3 – Simulation:

- I made a testbench and tried 5x5 multiplication with 16 bit width:

$$A = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 \\ 6 & 7 & 8 & 9 & 10 \\ 11 & 12 & 13 & 14 & 15 \\ 16 & 17 & 18 & 19 & 20 \\ 21 & 22 & 23 & 24 & 25 \end{bmatrix}$$

$$B = \begin{bmatrix} 26 & 27 & 28 & 29 & 30 \\ 31 & 32 & 33 & 34 & 35 \\ 36 & 37 & 38 & 39 & 40 \\ 41 & 42 & 43 & 44 & 45 \\ 46 & 47 & 48 & 49 & 50 \end{bmatrix}$$

It decimal result:

$$C = \begin{bmatrix} 590 & 605 & 620 & 635 & 650 \\ 1490 & 1530 & 1570 & 1610 & 1650 \\ 2390 & 2455 & 2520 & 2585 & 2650 \\ 3290 & 3380 & 3470 & 3560 & 3650 \\ 4190 & 4305 & 4420 & 4535 & 4650 \end{bmatrix}$$

What we expect on the waveform:

$$\begin{bmatrix} 0x24E & 0x25D & 0x26C & 0x27B & 0x28A \\ 0x5D2 & 0x5FA & 0x622 & 0x64A & 0x672 \\ 0x956 & 0x997 & 0x9D8 & 0xA19 & 0xA5A \\ 0xCD2 & 0xD34 & 0xD8E & 0xDE8 & 0xE42 \\ 0x105E & 0x10D1 & 0x1144 & 0x11B7 & 0x122A \end{bmatrix}$$

## Tb Code:

```
C: > Users > Sameh Fawzy > Desktop > yousefsameh_01288215640 > simu > systolic_array_tb.sv
1  module systolic_array_tb;
2      parameter DATAWIDTH = 16;
3      parameter N_SIZE = 5;
4
5      reg clk;
6      reg rst_n;
7      reg valid_in;
8      reg [N_SIZE*DATAWIDTH-1:0] matrix_a_in;
9      reg [N_SIZE*DATAWIDTH-1:0] matrix_b_in;
10     wire valid_out;
11     wire [N_SIZE*2*DATAWIDTH-1:0] matrix_c_out;
12
13     // DUT instantiation
14     systolic_array #(
15         .DATAWIDTH(DATAWIDTH),
16         .N_SIZE(N_SIZE)
17     ) dut (
18         .clk(clk),
19         .rst_n(rst_n),
20         .valid_in(valid_in),
21         .matrix_a_in(matrix_a_in),
22         .matrix_b_in(matrix_b_in),
23         .valid_out(valid_out),
24         .matrix_c_out(matrix_c_out)
25     );
26
27     // Clock generation
28     initial begin
29         clk = 0;
30         forever #1 clk = ~clk;
31     end
32
33
```

First we generate the clock.

```

initial begin
    rst_n = 0;
    valid_in = 0;
    @(negedge clk);
    rst_n = 1;
$display("Input Matrix A =");
$display(" Row 1 : 1  2  3  4  5");
$display(" Row 2 : 6  7  8  9 10");
$display(" Row 3 :11 12 13 14 15");
$display(" Row 4 :16 17 18 19 20");
$display(" Row 5 :21 22 23 24 25");
$display("Input Matrix B =");
$display(" Row 1 : 26 27 28 29 30");
$display(" Row 2 : 31 32 33 34 35");
$display(" Row 3 : 36 37 38 39 40");
$display(" Row 4 : 41 42 43 44 45");
$display(" Row 5 : 46 47 48 49 50");
    // Apply input rows (Matrix A and B as rows/columns)
    valid_in = 1;

    matrix_a_in = 80'h00150010000b00060001;
    matrix_b_in = 80'h001e001d001c001b001a;
    @(negedge clk);
    matrix_a_in = 80'h00160011000c00070002;
    matrix_b_in = 80'h0023002200210020001f;
    @(negedge clk);

    matrix_a_in = 80'h00170012000d00080003;
    matrix_b_in = 80'h00280027002600250024;
    @(negedge clk);

    matrix_a_in = 80'h00180013000e00090004;
    matrix_b_in = 80'h002d002c002b002a0029;
    @(negedge clk);

    matrix_a_in = 80'h00190014000f000a0005;
    matrix_b_in = 80'h003200310030002f002e;
    @(negedge clk);

```

**We enter matrix A and B as coloumns and rows.**

**Note: That we enter every row or coloumn from left to right and from down to up so the LSB in mata or b is the first element.**



```

        valid_in = 0;

        repeat(4) @(negedge clk);
        $display("output matrix C : ");
        $display("");
        $write("Row:1 ");
        for (int j = 0; j < N_SIZE; j++) begin
            $write("%0d ", matrix_c_out[j*DATAWIDTH*2 +: DATAWIDTH*2]);
        end
        $display("");

        @(negedge clk);
        $write("Row:3 ");
        for (int j = 0; j < N_SIZE; j++) begin
            $write("%0d ", matrix_c_out[j*DATAWIDTH*2 +: DATAWIDTH*2]);
        end
        $display("");

        @(negedge clk);
        $write("Row:3 ");
        for (int j = 0; j < N_SIZE; j++) begin
            $write("%0d ", matrix_c_out[j*DATAWIDTH*2 +: DATAWIDTH*2]);
        end
        $display("");

        @(negedge clk);
        $write("Row:4 ");
        for (int j = 0; j < N_SIZE; j++) begin
            $write("%0d ", matrix_c_out[j*DATAWIDTH*2 +: DATAWIDTH*2]);
        end
        $display("");

        @(negedge clk);
        $write("Row:5 ");
        for (int j = 0; j < N_SIZE; j++) begin
            $write("%0d ", matrix_c_out[j*DATAWIDTH*2 +: DATAWIDTH*2]);
        end
        $display("");
        $display("=== End of Output ===");
        $stop;
    end
endmodule

```


We then close the valid\_in and check the output every cycle and print it.

### Wave Form:




### First 2 rows



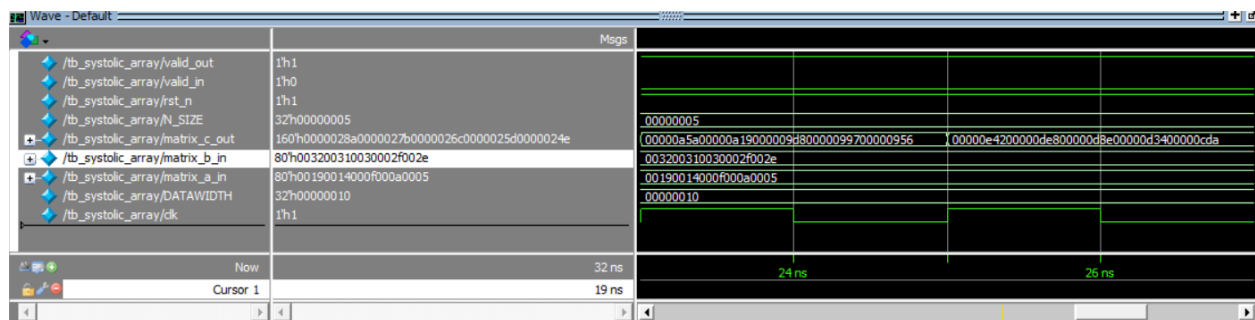

Last row

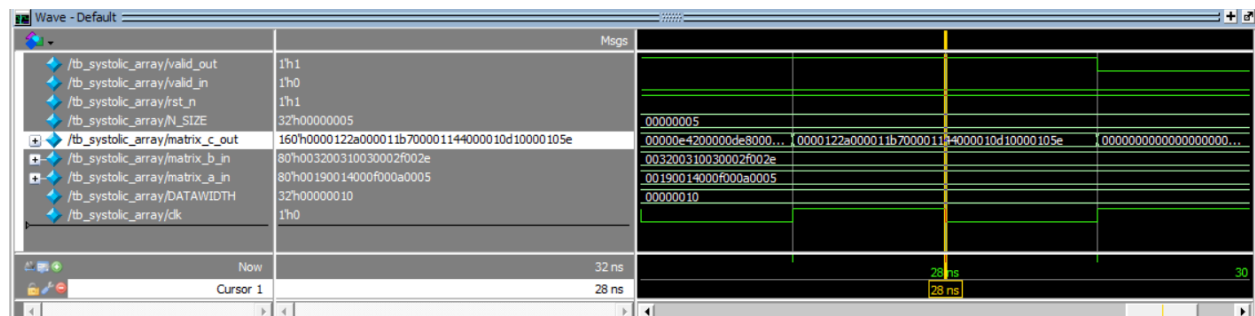

All are the values we expect.

Output in the transcript:

```
# Input Matrix A =
# Row 1 : 1 2 3 4 5
# Row 2 : 6 7 8 9 10
# Row 3 : 11 12 13 14 15
# Row 4 : 16 17 18 19 20
# Row 5 : 21 22 23 24 25
# Input Matrix B =
# Row 1 : 26 27 28 29 30
# Row 2 : 31 32 33 34 35
# Row 3 : 36 37 38 39 40
# Row 4 : 41 42 43 44 45
# Row 5 : 46 47 48 49 50
# output matrix C :
#
# Row:1 590 605 620 635 650
# Row:3 1490 1530 1570 1610 1650
# Row:3 2390 2455 2520 2585 2650
# Row:4 3290 3380 3470 3560 3650
# Row:5 4190 4305 4420 4535 4650
```

#### **4- What is missing?:**


I assumed valid\_in is like in the gif sent to us in the email and that it will take value 1 for N\_SIZE clk cycles then it will be 0 and wait for out. However, I contacted engineer Ahmed and he said that it is intended that valid\_in will be custom and randomly driven and that if it's 0 we will not take the input if it's 1 we will take it. This is not implemented in my code as I made it systematic to that the valid in will always be opened in the first cycles and will close at N\_size cycle.

We don't handle the case when for example we enter 2 inputs then valid\_in = 0 then we open it again , it will give wrong output.

To solve this problem I tried to stop the counter when valid\_in is low but it made a bigger problem with the output , if we find a way that when valid\_in = 0 the whole design will stop working then return from where it stopped , it will be solved.
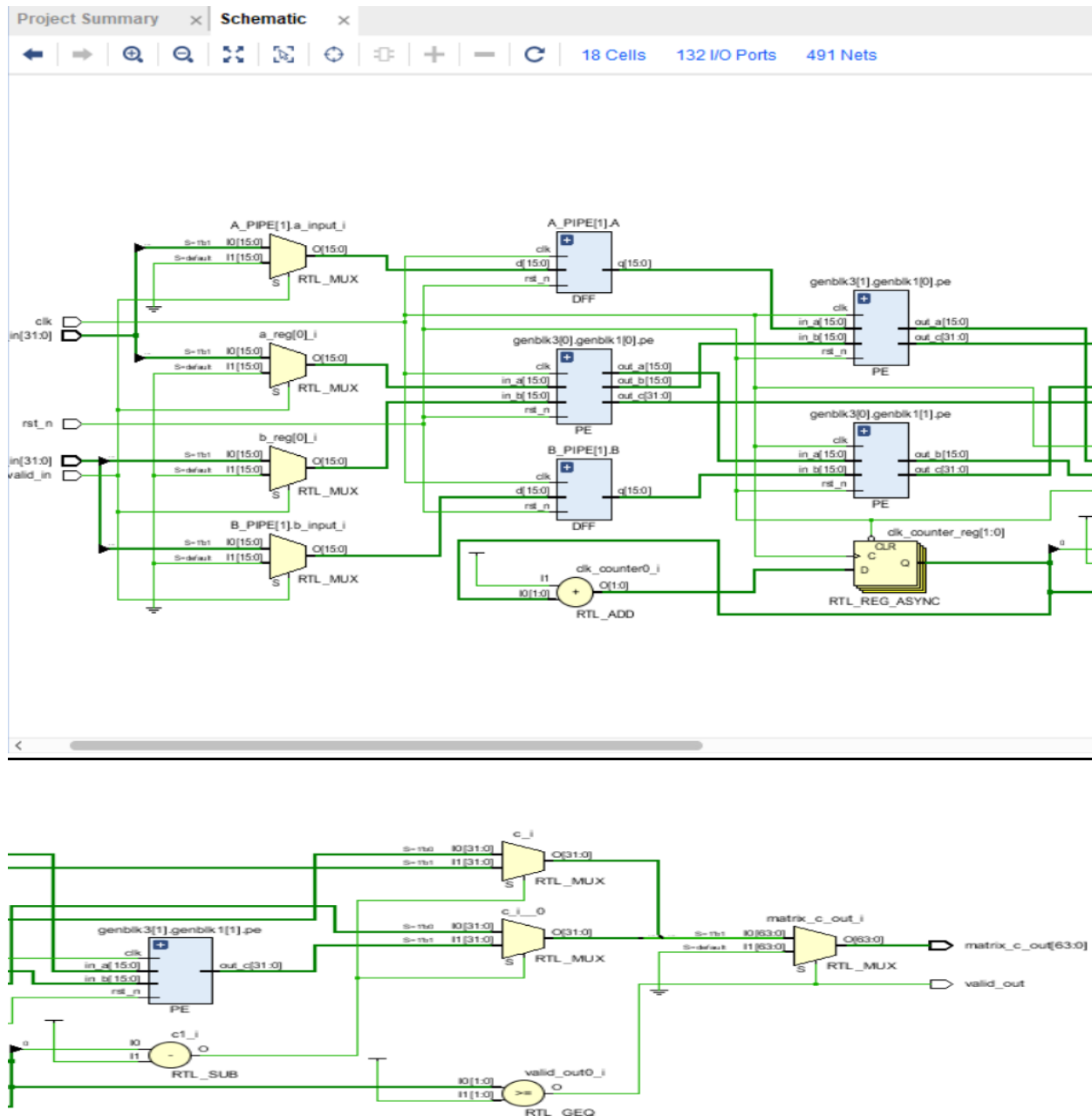
## 5- Vivado Elaboration Schematic:

Before I generated the schematic I made N\_SIZE = 2 so we can see it easily



For a 2x2 matrix multiplication we expect 4 PE blocks and 2 DFF and that's what we are seeing.